

No. of Printed Pages : 4

Roll No. ....

181031/171031/  
121031/31031

**3rd Sem. / Electronics & Communication Engg.**

**Subject : Electronic Devices & Circuits /**

**Analog Eltx. - II**

Time : 3 Hrs.

M.M. : 100

### SECTION-A

**Note:** Objective type questions. All questions are compulsory (10x1=10)

**(Course Outcome/CO)**

Q.1 RC Coupling is used for \_\_\_\_\_ amplification. (CO-304.1)

Q.2 The last stage of audio amplifier is called as \_\_\_\_\_ (CO-304.1)

Q.3 Class \_\_\_\_\_ power amplifier has highest collector efficiency. (CO-304.1)

Q.4 The negative feedback in amplifier increase \_\_\_\_\_ of its voltage gain. (CO-304.2)

Q.5 In a transistor oscillator, the active device is \_\_\_\_\_. (CO-304.2)

Q.6 Emitter follower is used for \_\_\_\_\_. (CO-304.2)

Q.7 Q factor of coil is \_\_\_\_\_. (CO-304.3)

(1)

181031/171031/  
121031/31031

Q.8 IC 555 timer has \_\_\_\_\_ Number of pin (CO-304.3)

Q.9 An ideal Op-Amp has \_\_\_\_\_ Input impedance. (CO-304.4)

Q.10 The output of 7805 IC and 7905 IC voltage regulator is \_\_\_\_\_ & \_\_\_\_\_ volt respectively. (CO-304.4)

### SECTION-B

**Note:** Very Short answer type questions. Attempt any ten parts out of twelve. 10x2=20

Q.11 Why the gain of amplifier is calculated in decibels? (CO-304.1)

Q.12 What do you mean by frequency response curve? (CO-304.1)

Q.13 What is the overall gain of multistage amplifier? (CO-304.1)

Q.14 List two advantages and disadvantages of push pull amplifier? (CO-304.1)

Q.15 What are the advantages of feedback amplifier? (CO-304.2)

Q.16 What is difference between oscillator and alternator? (CO-304.2)

(2)

181031/171031/  
121031/31031

- Q.17 Draw the block diagram of an oscillator?  
(CO-304.2)
- Q.18 Why RLC parallel circuit at resonance is also called as rejector circuit. (CO-304.2)
- Q.19 What is a clipping circuit? And also name its type. (CO-304.3)
- Q.20 What is an A-stable multi-vibrator? (CO-304.3)
- Q.21 Define slew rate. (CO-304.4)
- Q.22 How Op-Amp is used as inverting amplifier? (CO-304.4)

### SECTION-C

**Note:** Short answer type questions. Attempt any eight questions out of ten questions. (8x5=40)

- Q.23 Give the classification of amplifier depending upon various factors. (CO-304.1)
- Q.24 What are the advantages of push pull amplifier? (CO-304.1)
- Q.25 What is input offset voltage of an op-amp? (CO-304.4)
- Q.26 Describe working of emitter follower and its application. (CO-304.2)
- Q.27 Explain piezoelectric effect. (CO-304.2)

(3)

181031/171031/  
121031/31031

- Q.28 What is the condition for resonance in tuned amplifier? (CO-304.2)
- Q.29 How can we use op-amp as integrator? (CO-304.4)
- Q.30 Draw and explain the block diagram of IC 555 timer. (CO-304.3)
- Q.31 Explain the working of fixed voltage regulator IC 7805. (CO-304.3)
- Q.32 What are the applications of UPS? (CO-304.4)

### SECTION-D

**Note:** Long answer type questions. Attempt any three questions out of four. (3x10=30)

- Q.33 Explain working of SMPS with circuit diagram (CO-304.4)
- Q.34 What is clipping? Explain its types. (CO-304.3)
- Q.35 Explain with the help of diagram working of Wein bridge amplifier. (CO-304.2)
- Q.36 Explain push pull amplifier with diagram and why it is called push pull? (CO-304.1)

(**Note:** Course outcome/CO is for office use only)

(2400)

(4)

181031/171031/  
121031/31031

No. of Printed Pages : 4

Roll No. ....

121031/031031

**3rd Sem. / ECE / EE / MT / PE / ME**

**Subject : Analog Electronics - II**

Time : 3 Hrs.

M.M. : 100

### **SECTION-A**

**Note:** Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- a) Define decibel.
  - b) For RF frequencies, \_\_\_\_\_ coupling is used.
  - c) Efficiency of class B amplifier is \_\_\_\_\_.
  - d) What is use of heat sink.
  - e) Push pull amplifiers remove \_\_\_\_\_ distortion.
  - f) Gain of emitter follower is \_\_\_\_\_.
  - g) Define feedback.
  - h) With negative feedback, distortion in amplifier \_\_\_\_\_ (increases/decreases).

(1)

121031/031031

- i) Which type of feedback is used in oscillators.
- j) For oscillations the phase shift between output & input should be \_\_\_\_\_.
- k) Define resonance.
- l) What is impedance of series resonant circuit.
- m) Draw a ramp wave.
- n) The output of differentiator circuit is \_\_\_\_\_
- o) Define clipper circuit.
- p) Draw pin diagram of 7805.
- q) Expand CMRR.
- r) Define line resolution.

### **SECTION-B**

**Note:** Short answer type questions. Attempt any ten parts 10x4=40

- Q.2
- i) What is importance of impedance matching in amplifiers.
  - ii) What is cascading of amplifiers.

(2)

121031/031031

- iii) Why class A amplifiers are not used.
- iv) How negative feedback affects stability of amplifier.
- v) Draw different feedback topologies.
- vi) How can we make an amplifier into emitter follower circuit.
- vii) Explain piezo electric effect.
- viii) Draw & explain colpitts oscillator.
- ix) Draw a single tuned amplifier & its frequency response.
- x) Draw a tank circuit, derive its condition of resonance.
- xi) Draw & explain clamper circuit.
- xii) Show how IC 555 works as Monostable multivibrator.
- xiii) What are different characteristics of an ideal of Amp.
- xiv) Draw & explain schmitt trigger circuit.
- xv) Draw block diagram of D.C. regulated power supply.

(3)

121031/031031

## SECTION-C

**Note:** Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Draw and explain complementary symmetry push pull amplifier.
- Q.4 Explain in detail RC coupling in amplifiers.
- Q.5 Draw a neat diagram of wein's bridge oscillator, explain its working in detail.
- Q.6 Draw circuit diagram of bistable multivibrator, explain its operation.
- Q.7 Write short notes on following.
  - i) opAmp as adder, subtractor
  - ii) SMPS

(2660)

(4)

121031/031031

No. of Printed Pages : 4

Roll No. ....

121031/031301

**3rd Sem. / ECE / Med Eltx.**

**Subject : Analog Electronics-II**

Time : 3 Hrs.

M.M. : 100

### **SECTION-A**

**Note:** Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- a) Define Multistage amplifier.
  - b) Define Impedance matching.
  - c) Draw input/output waveforms for Class 'C' power amplifier.
  - d) Efficiency of class C amplifier is \_\_\_\_\_ than that of class A amplifier.
  - e) What is the function of heat sink?
  - f) Define heat dissipation curve.
  - g) What is frequency response curve?
  - h) Positive feedback is used in \_\_\_\_\_.
  - i) Define sinusoidal Oscillators.

(1)

121031/031301

- j) Name any two essential components of oscillator.
- k) Negative feedback is used in Oscillator. (True/ False)
- l) Explain Barkhausen criteria for oscillations.
- m) Define bandwidth of resonant circuit.
- n) Draw any two wave shapes.
- o) Define bistable multivibrator.
- p) Expand PSRR.
- q) Which IC is used as voltage regulator?
- r) Explain line regulation.

### **SECTION-B**

**Note:** Short answer type questions. Attempt any ten parts 10x4=40

- Q.2
- i) What is the gain multistage amplifier?
  - ii) Compare transformer coupled and direct coupled amplifier.
  - iii) What is importance of impedance matching in amplifiers?

(2)

121031/031301

- iv) Draw the block diagram of IC 555.
- v) Explain working of single ended power amplifier.
- vi) Draw diagram of RC coupled amplifier without emitter bypass capacitor.
- vii) Explain effect of negative feedback on stability.
- viii) Explain block diagram of sinusoidal oscillator.
- ix) Explain the tuned collector oscillator.
- x) Write a short note on "Parallel resonant circuit".
- xi) Write short note on "RL integrating circuits".
- xii) Describe the operation of transistor as switch.
- xiii) Write applications of astable multivibrators.
- xiv) What are characteristics of ideal operational amplifier?
- xv) Explain concept of DC power supply.

## SECTION-C

**Note:** Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Explain diagram of Complementary symmetry Push Pull amplifier. What are advantages of complementary push pull amplifiers.
- Q.4 What is effect of negative feedback on distortion of an amplifier? Explain in detail.
- Q.5 Explain double tuned voltage amplifier and their frequency response characteristics.
- Q.6 What is an operational amplifier? Explain basic operational amplifier as scale changer and Integrator.
- Q.7 Explain diagram and working of SMPS.

No. of Printed Pages : 4

Roll No. ....

121031/031301

**3rd Sem. / ECE / Med Eltx.**

**Subject : Analog Electronics-II**

Time : 3 Hrs.

M.M. : 100

### **SECTION-A**

**Note:** Very Short Answer type questions. Attempt any 15 parts. (15x2=30)

- Q.1
- a) Define Multistage amplifier.
  - b) Define Impedance matching.
  - c) Draw input/output waveforms for Class 'C' power amplifier.
  - d) Efficiency of class C amplifier is \_\_\_\_\_ than that of class A amplifier.
  - e) What is the function of heat sink?
  - f) Define heat dissipation curve.
  - g) What is frequency response curve?
  - h) Positive feedback is used in \_\_\_\_\_.
  - i) Define sinusoidal Oscillators.

(1)

121031/031301

- j) Name any two essential components of oscillator.
- k) Negative feedback is used in Oscillator. (True/ False)
- l) Explain Barkhausen criteria for oscillations.
- m) Define bandwidth of resonant circuit.
- n) Draw any two wave shapes.
- o) Define bistable multivibrator.
- p) Expand PSRR.
- q) Which IC is used as voltage regulator?
- r) Explain line regulation.

### **SECTION-B**

**Note:** Short answer type questions. Attempt any ten parts 10x4=40

- Q.2
- i) What is the gain multistage amplifier?
  - ii) Compare transformer coupled and direct coupled amplifier.
  - iii) What is importance of impedance matching in amplifiers?

(2)

121031/031301

- iv) Draw the block diagram of IC 555.
- v) Explain working of single ended power amplifier.
- vi) Draw diagram of RC coupled amplifier without emitter bypass capacitor.
- vii) Explain effect of negative feedback on stability.
- viii) Explain block diagram of sinusoidal oscillator.
- ix) Explain the tuned collector oscillator.
- x) Write a short note on "Parallel resonant circuit".
- xi) Write short note on "RL integrating circuits".
- xii) Describe the operation of transistor as switch.
- xiii) Write applications of astable multivibrators.
- xiv) What are characteristics of ideal operational amplifier?
- xv) Explain concept of DC power supply.

## SECTION-C

**Note:** Long answer type questions. Attempt any three questions. 3x10=30

- Q.3 Explain diagram of Complementary symmetry Push Pull amplifier. What are advantages of complementary push pull amplifiers.
- Q.4 What is effect of negative feedback on distortion of an amplifier? Explain in detail.
- Q.5 Explain double tuned voltage amplifier and their frequency response characteristics.
- Q.6 What is an operational amplifier? Explain basic operational amplifier as scale changer and Integrator.
- Q.7 Explain diagram and working of SMPS.